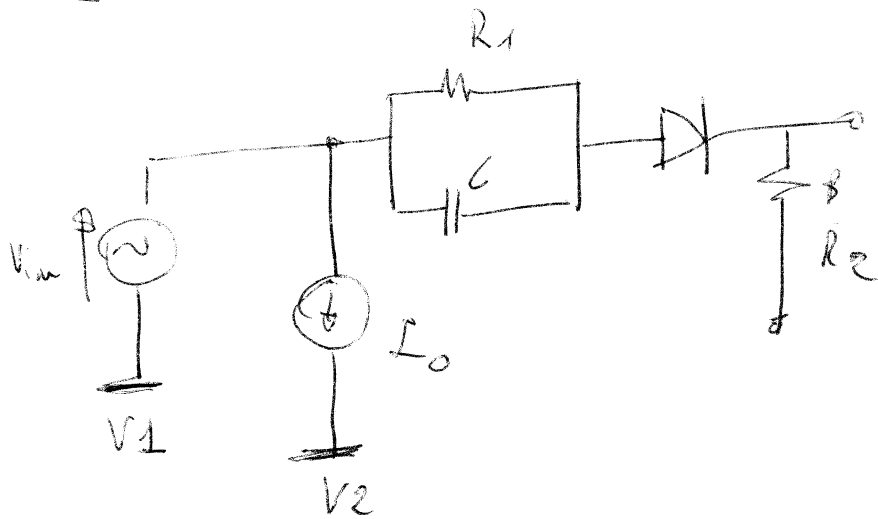


①



$$R_1 = R_L = 1 \text{ k}\Omega$$

$$C = 1 \text{ pF}$$

$$I_0 = 1 \text{ mA}$$


$$V_D = 3 \text{ V}$$

$$0 \leq V_1 \leq 8 \text{ V}$$

1) v_{out} in funzione di V_1

2) Per $V_1 = 5 \text{ V}$ disegnare il grafico di piccolo segnale e $v_{out}/v_{in}(s)$

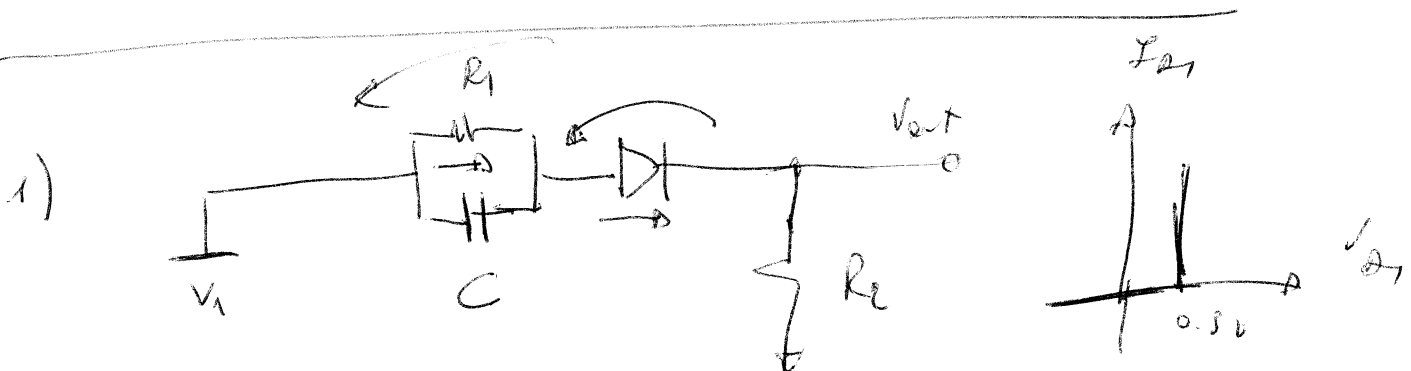3) Per $V_1 = 5 \text{ V}$ Diagrammi di Bode



Notes: $I_{D1} > 0$
 $V_{D1} = V_D = 0.5 \text{ V}$


$$\begin{cases} I_{D1} = v_{out} / R_L \\ v_{out} = V_1 - R_1 I_{D1} - V_D \end{cases}$$

$$I_{D1} = \frac{V_1 - R_1 I_{D1} - V_f}{R_2} (> 0)$$

$$I_{D1} = \frac{V_1}{R_2} - \frac{V_f}{R_2} - \frac{R_1}{R_2} I_{D1}$$




$$V_{out} = \frac{1}{2} (V_1 - 0.5)$$

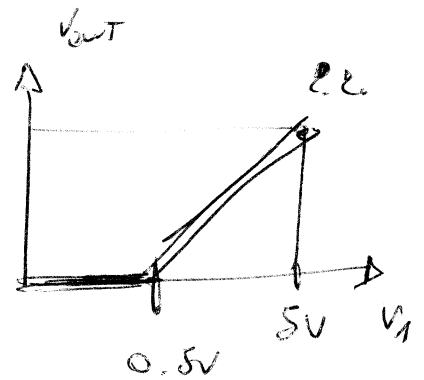

$$I_{D1} = \frac{V_1 - V_f}{R} > 0 \Rightarrow V_1 > V_f \text{ DI ON}$$

$$V_1 < V_f \text{ DI OFF}$$

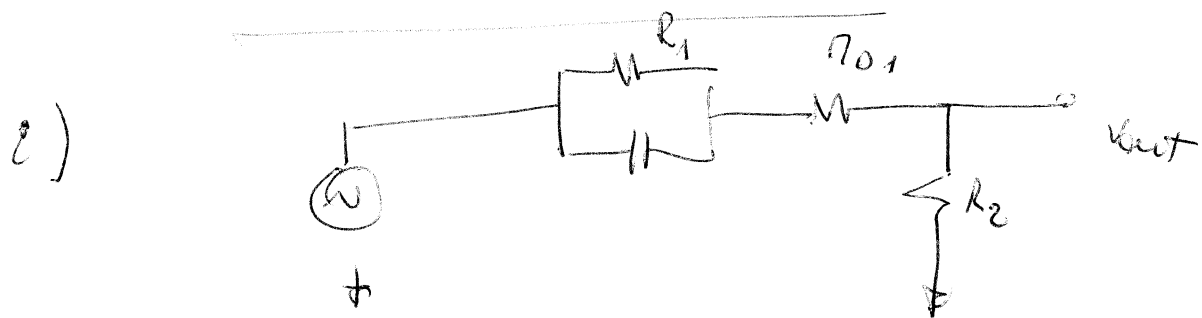

$$I_{D1} = 2.25 \text{ mA per } V_1 = 5 \text{ V}$$

$$I_{in} = \frac{I_{out}}{V} (1/R)$$


$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_2 + r_{D1} + R_1 \parallel \frac{1}{sC}} = \frac{R_2}{R_2 + r_{D1} + \frac{R_1}{1+sCR_1}} =$$


$$= \frac{R_2}{R_2 + r_{D1} + R_1} \cdot \frac{1}{1+sCR_1 \parallel (r_{D1} + R_2)}$$

$$\tau = C (R_c \parallel (R_1 + a_{v1})) = 29 \text{ ns} \quad (5.3 \text{ MHz})$$

②

3) Diagramm d. Bode

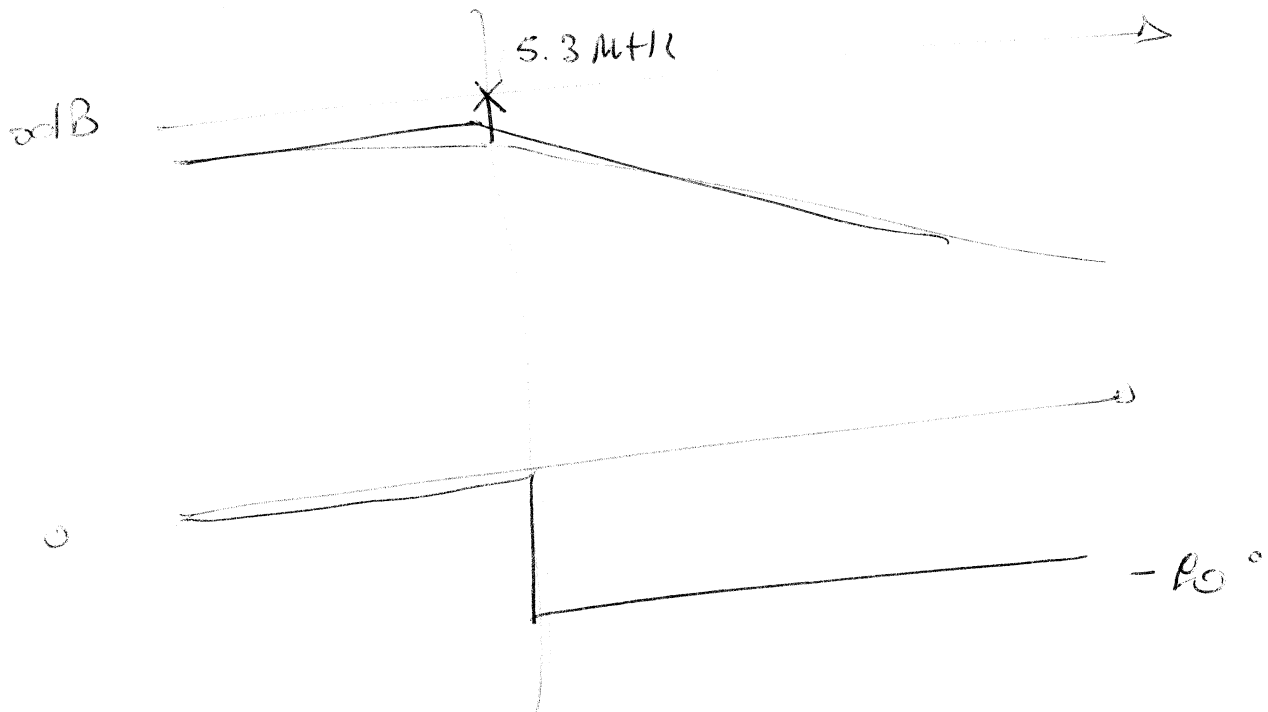

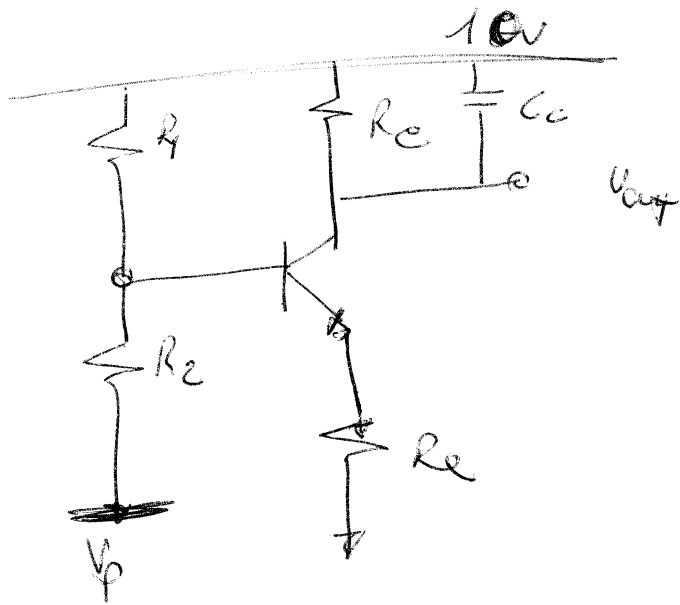

$$\beta = 400$$

(1)

$$A_{in} = \infty$$

$$R_1 = R_2 = 1\text{ M}\Omega$$

$$R_E = 1\text{ k}\Omega$$

$$R_C = 3\text{ k}\Omega$$

$$C_C = 10\text{ }\mu\text{F}$$

$$V_1 = 10\text{ V}$$

$$V_D = 1\text{ V}$$


1. Punto op.

2. v_{out}/v_{in}


3. Diagramma di Bode

4. ~~Calcolare~~ VALORE LIMITE di R_E che mantiene il bipolo in zona attiva diretta

1) P_{op}

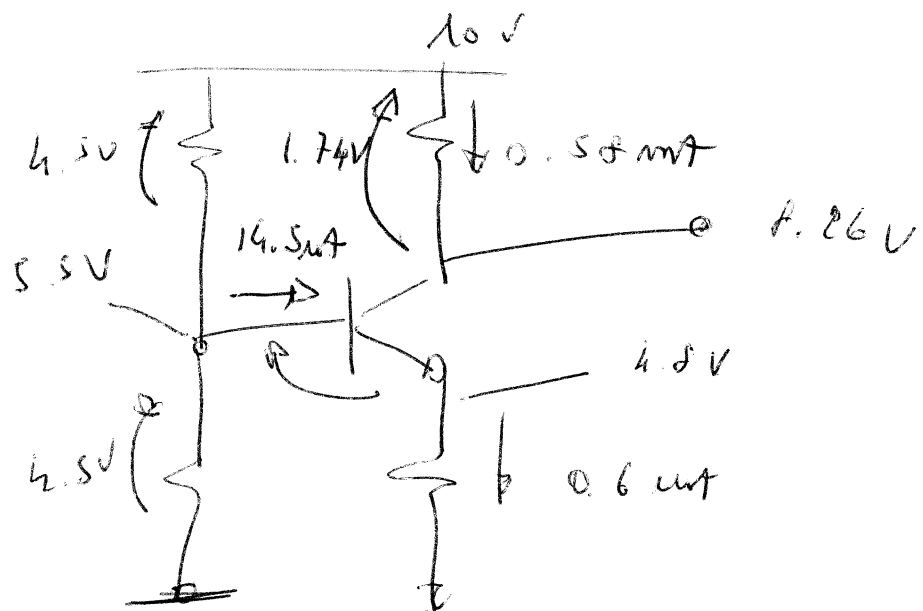

2. V_{out}/V_{in} .

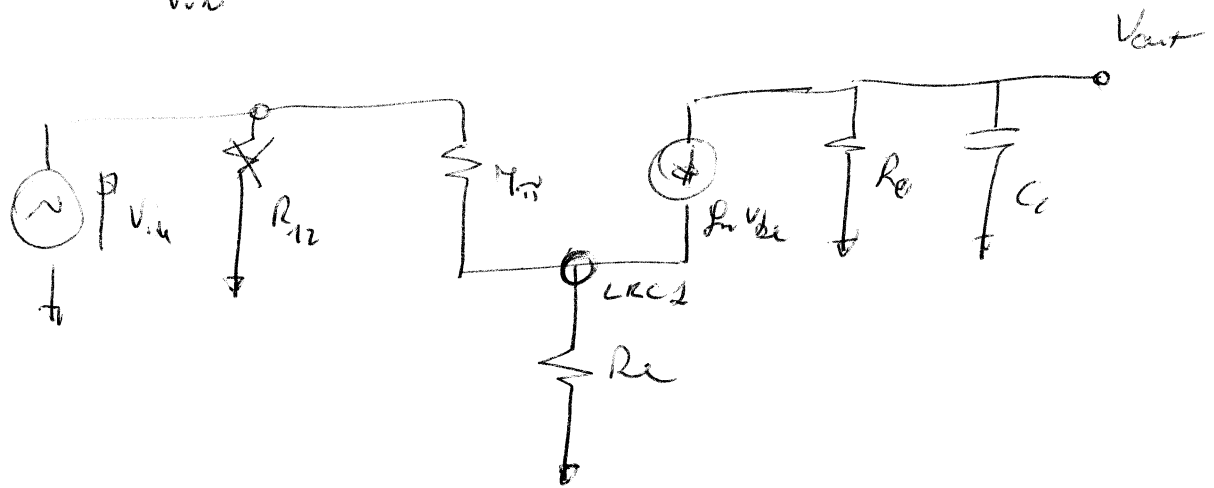

$$- V_{out} = - i_{c0} \frac{R_c}{1 + s C_c R_c} = - \beta V_{be} \cdot \frac{R_c}{1 + s C_c R_c}$$

$$\begin{cases} V_{be} = V_{in} - V_e \\ \frac{V_{be}}{r_{\pi}} + \beta V_{be} = \frac{V_e}{R_e} \quad (\text{KCL}) \end{cases}$$

$$(V_{in} - V_e) \left(\frac{1}{r_{\pi}} + \beta \right) = \frac{V_e}{R_e}$$

$$V_{in} \left(\frac{1}{r_{\pi}} + \beta \right) = V_e \left(\frac{1}{R_e} + \frac{1}{r_{\pi}} + \beta \right)$$

$$V_e = \frac{\frac{1}{r_{\pi}} + \beta}{\frac{1}{R_e} + \frac{1}{r_{\pi}} + \beta} V_{in}$$

$$V_{be} = V_{in} - V_e = \frac{\frac{1}{R_e}}{\frac{1}{R_e} + \frac{1}{r_o} + g_m} V_{in} \quad (2)$$

$$= \frac{\pi_{\pi}}{\pi_{\pi} + R_e + \frac{\beta}{g_m} g_m R_e} V_{in} \approx$$

$$= \frac{\pi_{\pi}}{\pi_{\pi} + \beta R_e} \approx \frac{\frac{1}{g_m} \frac{1}{R_e}}{\frac{1}{g_m} + R_e} V_{in} =$$

$$= \frac{\cancel{g_m R_e} V_{in}}{1 + g_m R_e}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m R_e}{1 + g_m R_e} \cdot \frac{1}{1 + s C_e R_e}$$


$$r_o = 1.72 \text{ k}\Omega$$

$$g_m = 83.2 \text{ mA/V} \quad (43 \text{ }\Omega)$$

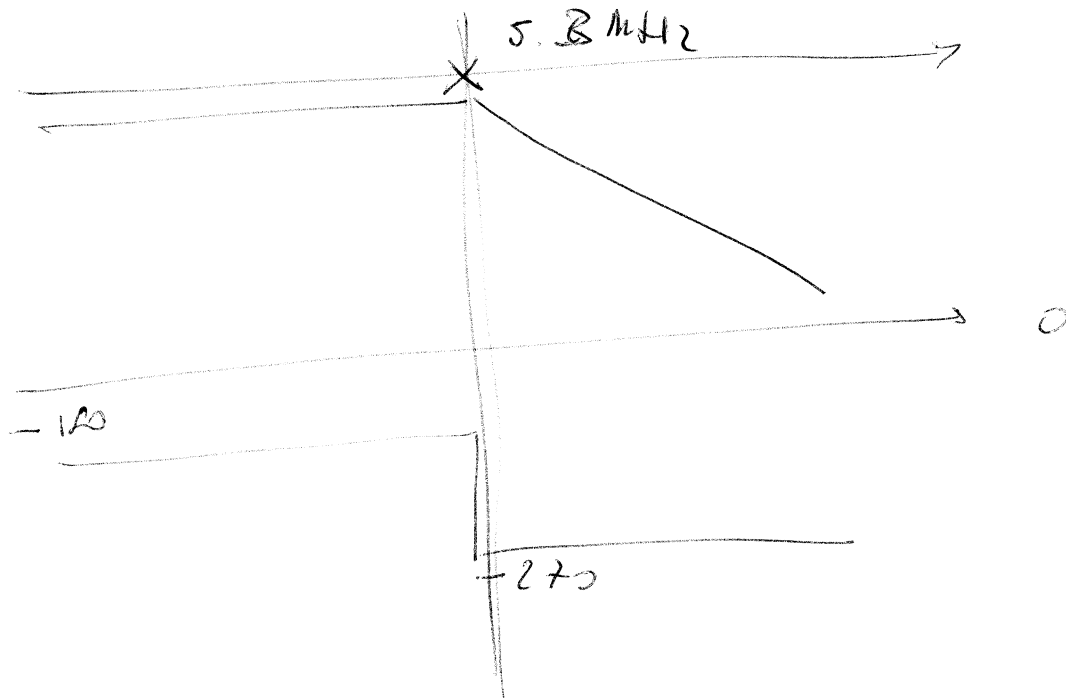
3) BODE

$$\tau_c = R_c \cdot C_c = 30 \mu s \quad (5.3 \text{ MHz})$$

$$-\frac{R_c}{R_E} = 0.37 \quad (-\text{dB})$$




4) VALORE LIMITE DI R_c

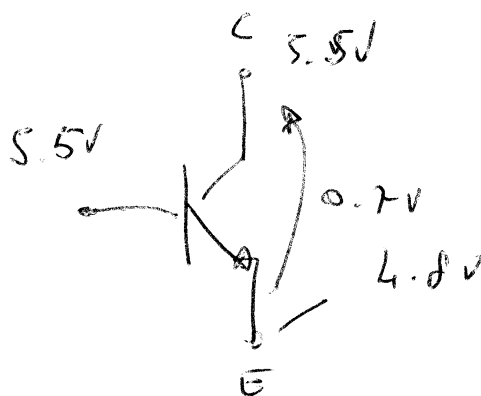

$$V_{CE} > 0 = V_C - V_E = (V_{CC} - R_c I_C) - 4.8V =$$

$$= (10 - R_c \cdot 0.5 \text{ mA}) - 4.8V > 0 \Rightarrow$$
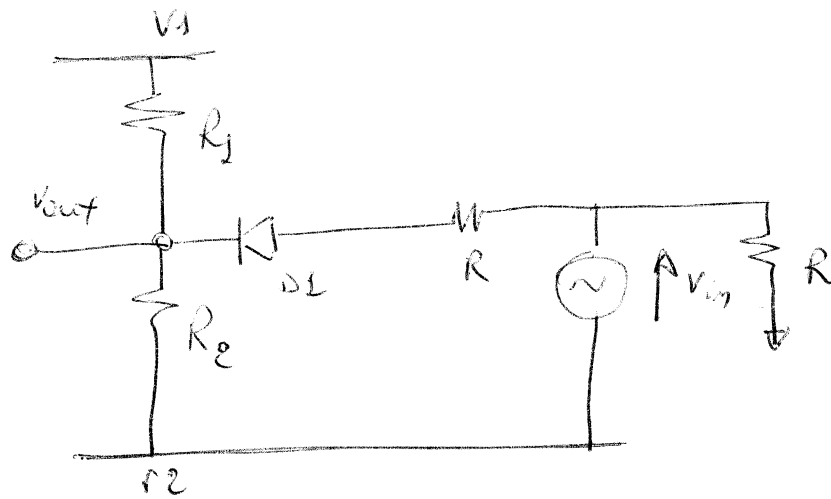
$$\Rightarrow R_c < \frac{4.8V}{0.5 \text{ mA}} = 7.75 \text{ k}\Omega$$




$$V_1 = 0V \div 5V \quad (1)$$

$$R_1 = R_2 = R = 1k\Omega$$

$$V_2 = 2V$$

$$V_f = 0.7$$

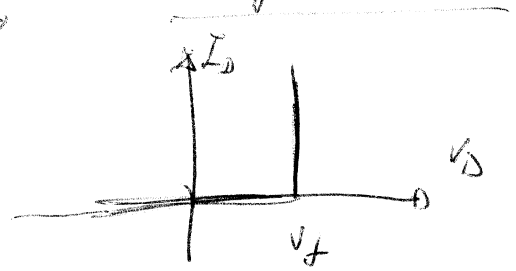


1) I_{D1} per V_1 tra 0V e 5V

2) Per $V_1 = 0V$ si calcol $\frac{v_{out}}{v_{lim}}$

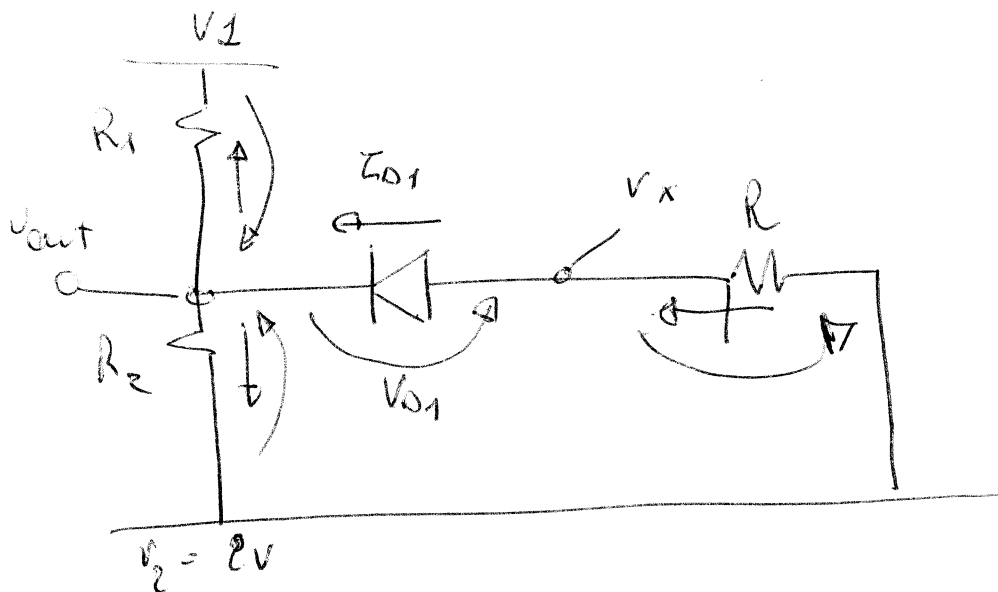1) Ipotesi di 0000 0V

$$\begin{cases} I_{D1} > 0 \\ V_{D1} = V_f = 0.7V \end{cases}$$



$$\begin{cases} I_{D1} = I_{R1} + I_{R2} = \frac{v_{out} - V_1}{R_1} + \frac{v_{out} - V_2}{R_2} > 0 \\ v_{out} = v_x - V_f \\ v_x = V_2 - R I_{D1} \end{cases}$$

$$\begin{cases} V_{out} = (V_2 - R I_{D1}) - V_f \\ I_{D1} = \frac{V_{out} - V_1}{R_1} + \frac{V_{out} - V_2}{R_2} \end{cases}$$

$$R_1 = R_2 = R$$


$$I_{D1} = \frac{V_2 - R I_{D1} - V_f - V_1}{R_1} + \frac{V_2 - R I_{D1} - V_f - V_2}{R_2}$$

$$3 I_{D1} = \cancel{V_2} + \cancel{V_2} - V_1$$

$$I_{D1} = 2 \frac{V_{out}}{R} - \frac{V_1 + V_2}{R} =$$

$$= 2 \frac{V_2}{R} - \frac{R I_{D1}}{R} - 2 \frac{V_f}{R} - \frac{V_1 + V_2}{R} \Rightarrow$$
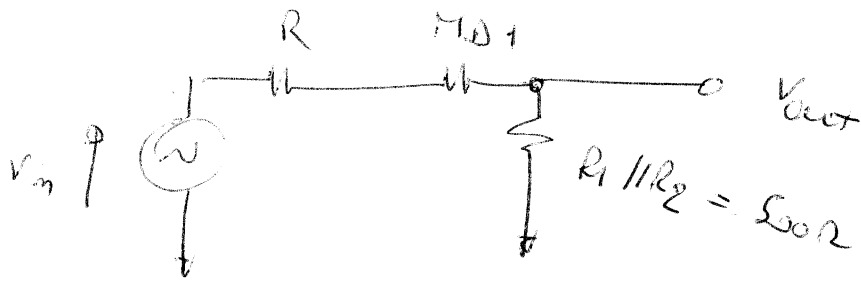
$$\Rightarrow 3 I_{D1} = \frac{V_2}{R} - 2 \frac{V_f}{R} - \frac{V_1}{R} > 0$$



$$\frac{v_{out}}{v_{in}} = \frac{R_{L2}}{R_{L2} + R + M_{D1}} = \frac{R/2}{\frac{3}{2}R + \frac{1}{g_{mD1}}}$$

$$I_{D1} = \frac{V_2 - 2V_f - V_1}{3R} > 0$$


$$V_1 < V_2 - 2V_f = 2 - 2 \times 0.7 = 0.6$$

D1 ON

$$V_1 \geq 0.6 \quad \Rightarrow \quad \text{D1 OFF}$$

Curve I_{D1} vs V_1

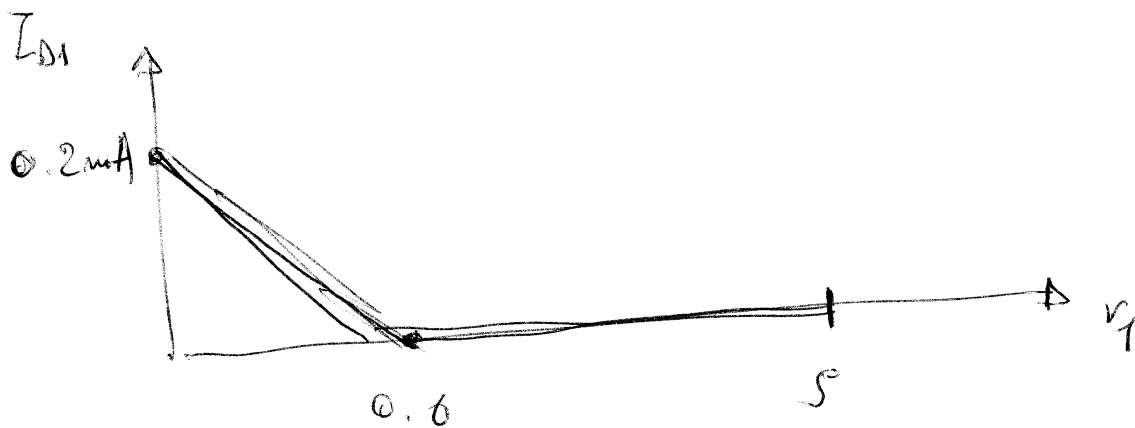
$$I_{D1} = \frac{1}{3} (0.6 - V_1) \text{ mA}$$



2) V_{out}/V_{in} per $V_1 = 0V$

$$g_{mns} = \frac{I_{D1}}{V_{th}} = \frac{0.2 \text{ mA}}{28 \text{ mV}} = 7.14 \text{ mA/V} \quad (125 \Omega)$$

①

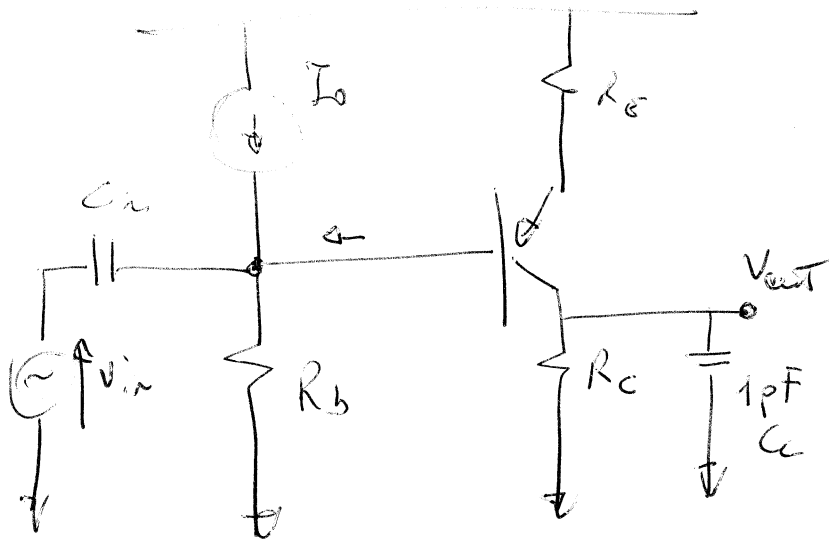

$$\beta = 100$$

$$R_b = 2.3 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega$$

$$R_C = 1.2 \text{ k}\Omega$$

$$I_C = 1 \text{ mA}$$

$$C_{in} = 1 \text{ mF}$$


$$C_E = 1 \text{ pF}$$

1) Punto OP

2) V_{out}/V_{in} (dB)

3) MAX R_C che mantiene il bipolare in saturazione

1) Punto OP

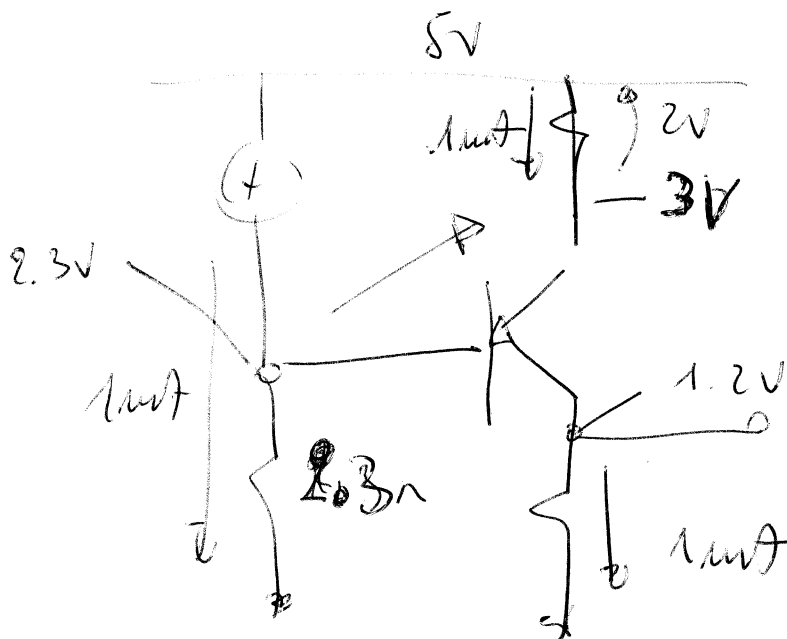

MEGA EQUATIONS:

$$I_C = \frac{V_B}{R_b} - I_{BA}$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E = \frac{V_{DD} - V_E}{R_E}$$



$$V_B - V_E = 0.7$$

$$1.8 \text{ V}$$

$$I_C = \frac{V_B}{R_b} - \frac{5 - V_B - 0.7}{(\beta + 1) R_E}$$

c) Riccolo Equival

2

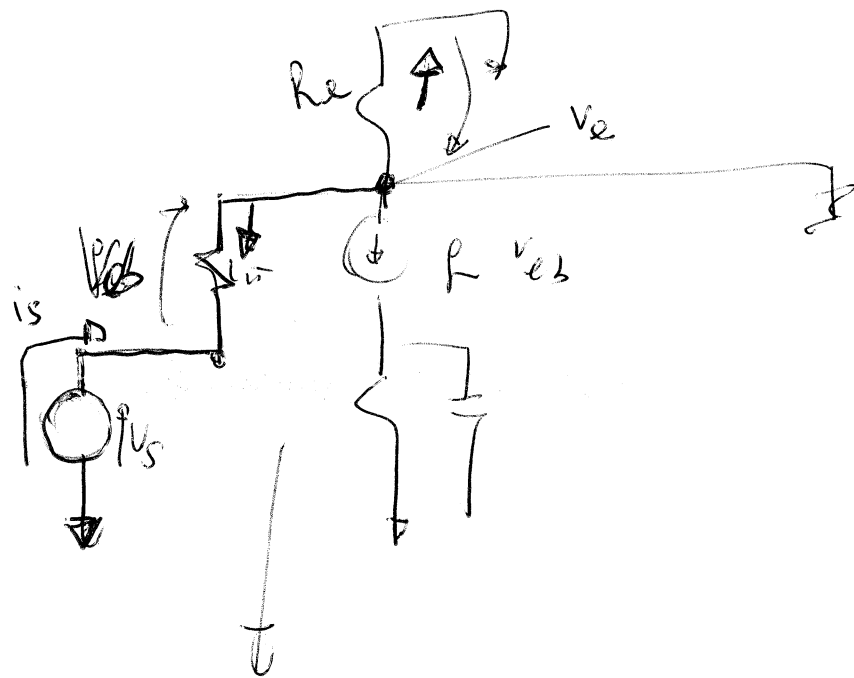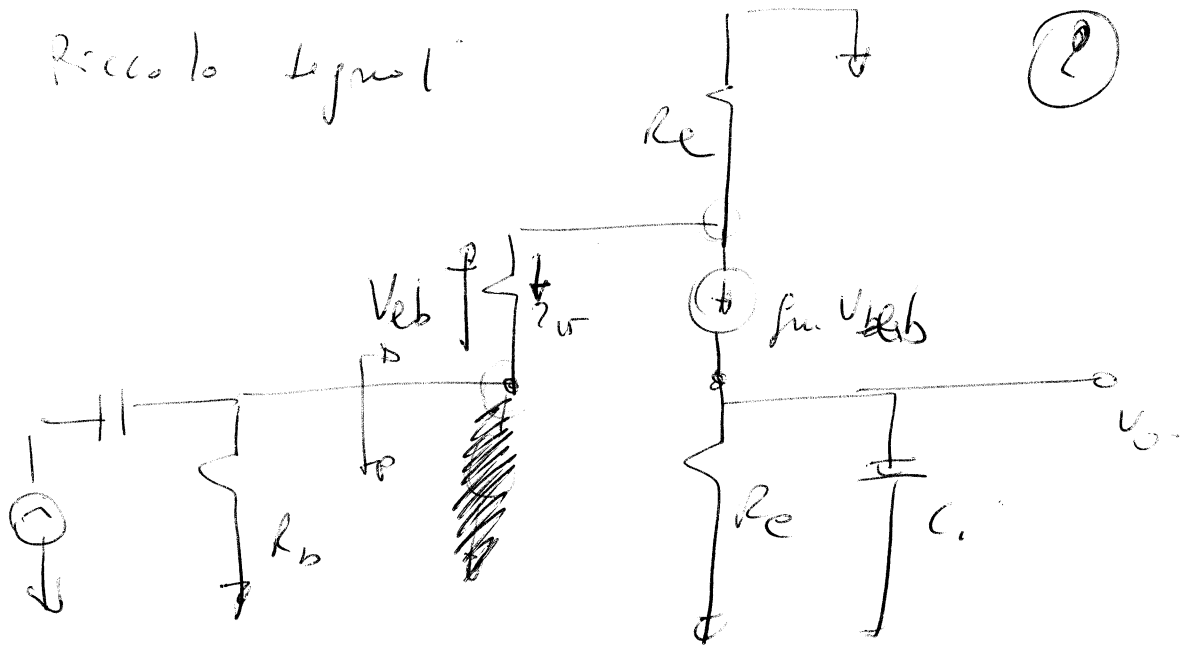

$$\frac{v_{eb}}{r_{\pi}} + \beta i_b + \frac{v_e}{R_e} = 0$$


$$v_{eb} = v_e - v_s$$

$$i_s = -\frac{v_{eb}}{r_{\pi}}$$

$$-i_s + \beta r_{\pi} i_s + \frac{v_{eb} + v_s}{R_e} = 0 \implies$$

~~$$i_s (1 + \beta r_{\pi}) + \frac{v_{eb} + v_s}{R_e} = 0$$~~
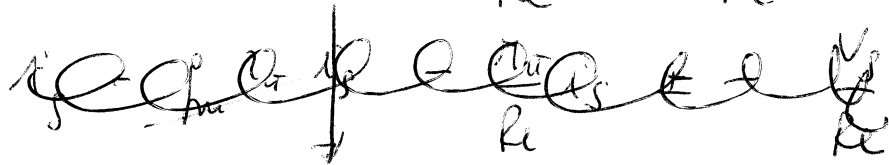
$$-i_s - \beta_m \gamma_{\pi} i_s - \frac{\gamma_{\pi}}{R_e} i_s + \frac{V_s}{R_e} = 0$$



(3)

$$\frac{V_s}{R_e} = R_e \left(1 + \beta_m \gamma_{\pi} + \frac{\gamma_{\pi}}{R_e} \right) i_s$$

$$i_s = -\frac{V_{eb}}{r_{\pi}} \quad V_{eb} = -\beta_{\pi} i_s$$

$$\frac{V_{eb}}{r_{\pi}} + \beta_m V_{eb} + \frac{V_e}{R_e} = 0$$

$$V_{eb} = V_e - V_s$$

$$-i_s - \beta_m \gamma_{\pi} i_s + \frac{V_{eb} + V_s}{R_e} = 0$$

$$-i_s + \beta_m \gamma_{\pi} i_s + \frac{\gamma_{\pi}}{R_e} i_s = \frac{V_s}{R_e}$$

$$\frac{V_s}{R_e} = R_e + \gamma_{\pi} + \beta_m \gamma_{\pi} R_e$$

$$= R_e \left(1 + \beta_m \gamma_{\pi} \right) + \gamma_{\pi} =$$

$$\approx \left(3R_e + \frac{\beta}{\beta_m} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{2.27 \mu s (70 kHz)}{s C_{in} R^1}}{1 + s C_{in} R^1} \cdot \frac{g_m R_E}{1 + g_m R_E} \cdot \frac{1}{1 + s C_E R_E}$$

(4)


$$R^1 = R_b \parallel \left(3 R_E + \frac{3}{g_m} \right)$$

$202.5 nR$


$1.2 ms$
(132.6 kHz)

3) Dim R_C in modo da avere $+3dB$ — $[R_C = 2]$

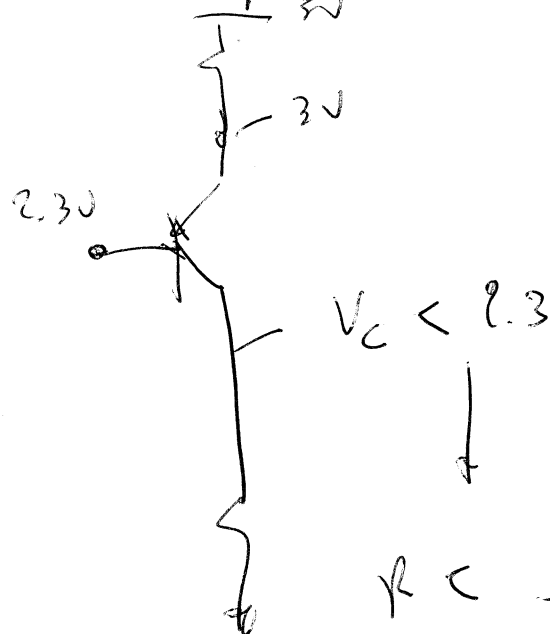
4) Dim R_C per mettere Q_1 in zona attiva



$$R < \frac{2.3}{1 mA} = 2.3 nR$$

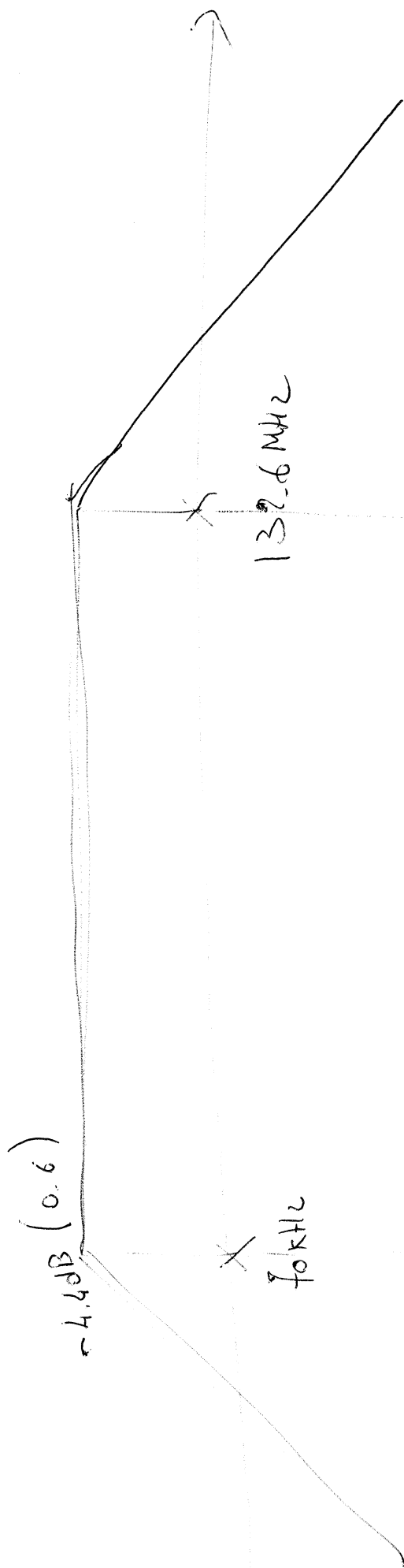

270
 -90

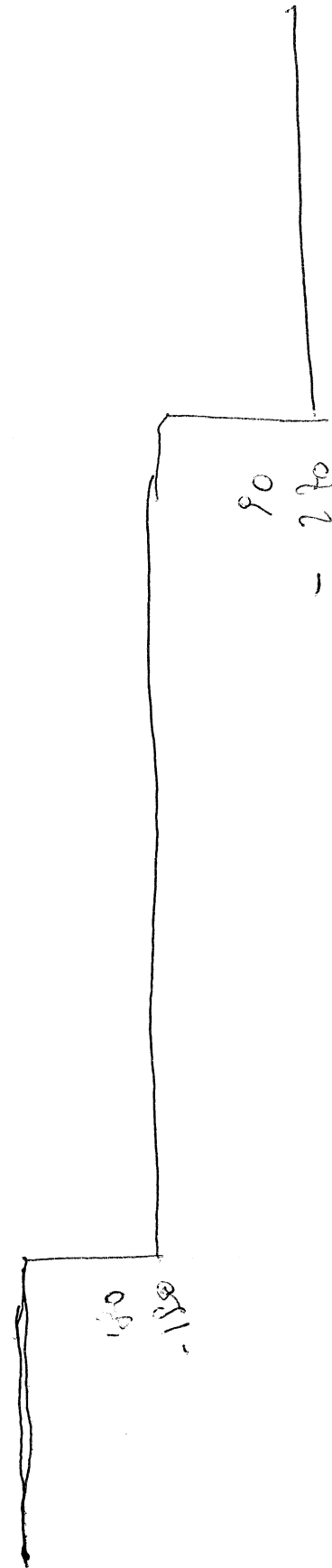

5